

Analog Electronics

Course No: AE-2

Lec: Oscillator

Course Instructors:




Dr. A. Roy



Department of ECE, PDEU

Positive Feedback

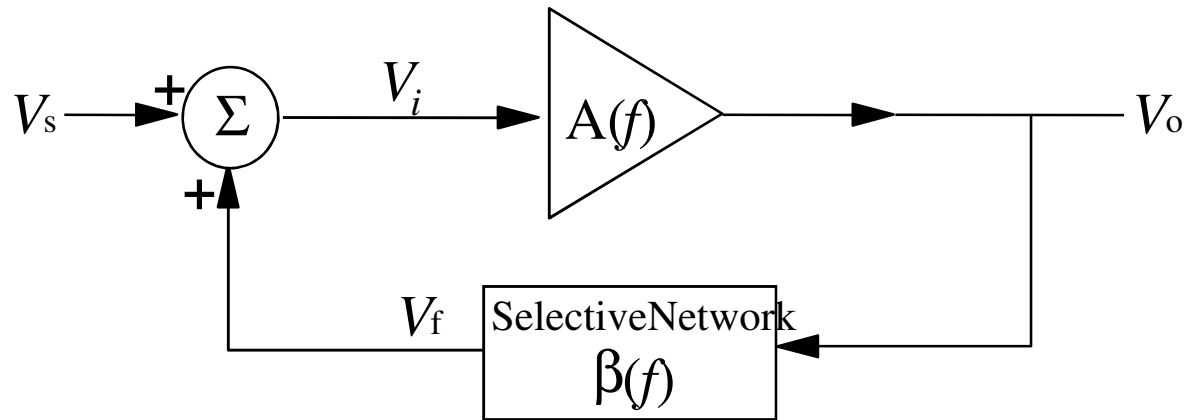- When input and feedback signal both are in same phase, It is called a positive feedback.
- Positive feedback is used in analog and digital systems.
- A primary use of +ve feedback is in the production of oscillators.



$$V_o = AV_i = A(V_s + V_f) \quad \text{and} \quad V_f = \beta V_o$$

$$\frac{V_o}{V_s} = \frac{A}{1 - A\beta}$$

Barkhausen Criterion: for oscillator $\beta A=1$ and +ve feedback

Oscillator Circuit

- Oscillator is an electronic circuit which converts dc signal into ac signal.
- Oscillator is basically a positive feedback amplifier with unity loop gain.
- For an inverting amplifier- feedback network provides a phase shift of 180° while for non-inverting amplifier- feedback network provides a phase shift of 0° to get positive feedback .

$$\frac{V_o}{V_s} = \frac{A}{1 - A\beta}$$

If $\beta A = 1$ then $V_o = \infty$; Very high output with zero input.


Use positive feedback through frequency-selective feedback network to ensure sustained oscillation at ω_o

Use of Oscillator Circuits

- ❖ Clock input for CPU, DSP chips ...
- ❖ Local oscillator for radio receivers, mobile receivers, etc
- ❖ As a signal generators in the lab
- ❖ Clock input for analog-digital and digital-analog converters

Oscillators

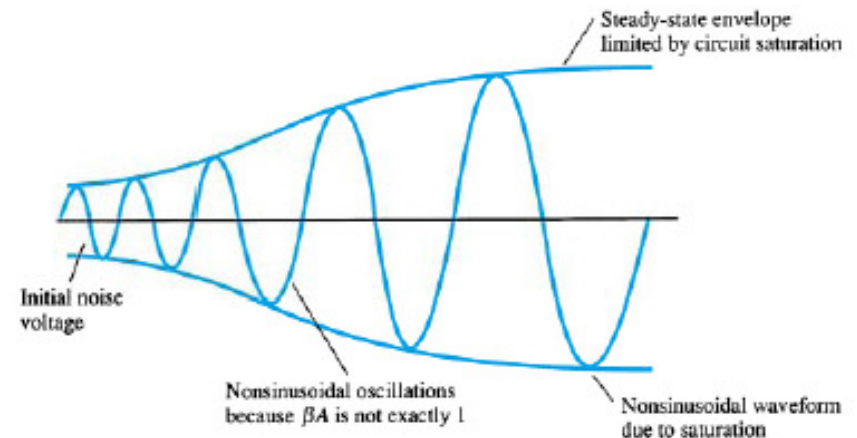- If the feedback signal is not positive and gain is less than unity, oscillations dampen out.
- If the gain is higher than unity then oscillation saturates.




Type of Oscillators

Oscillators can be categorized according to the types of feedback network used:

- RC Oscillators: Phase shift and Wien Bridge Oscillators
- LC Oscillators: Colpitt and Hartley Oscillators
- Crystal Oscillators

RC Oscillators

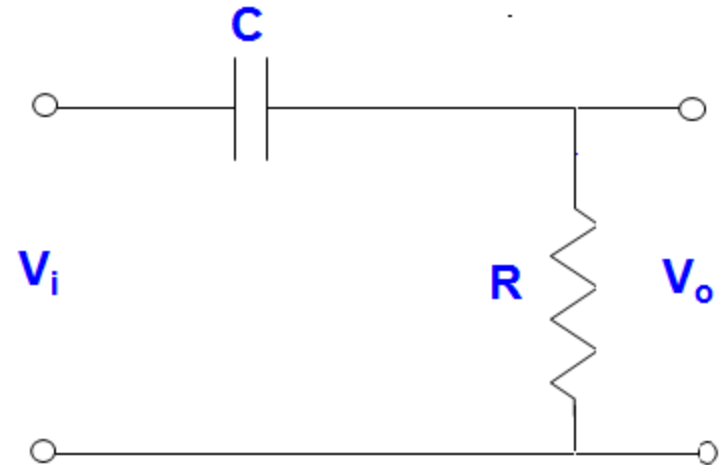
$$V_o = \left(\frac{R}{R - jX_c} \right) V_{in} \quad \text{and} \quad \phi = \tan^{-1} \left(\frac{X_c}{R} \right)$$



- $\Phi = 0^\circ$ if $X_c = 0$ and $\Phi = 90^\circ$ if $R = 0$
- However adjusting R to zero is impractical because it would lead to no voltage across R , thus in a RC circuit, phase shift is always $\leq 90^\circ$ and it is a function of frequency.
- Hence to get 180° phase shift from the feedback network, we need 3 RC circuits.
- RC oscillators build by using inverting amplifier and 3 RC circuits is known as phase shift oscillator.

RC Oscillators: Phase shift Oscillator

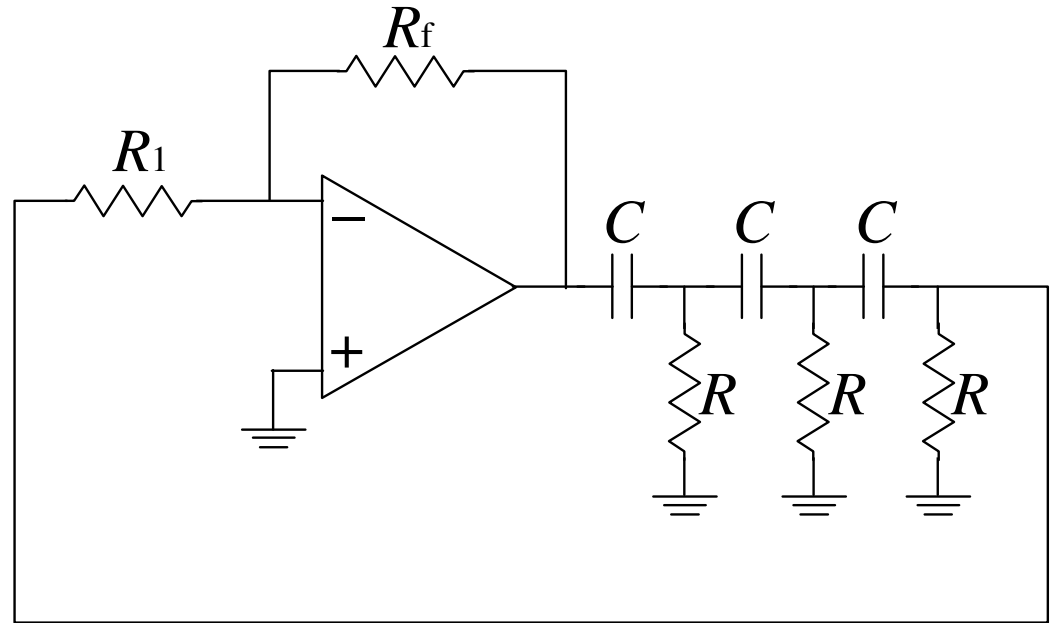- Use of an inverting amplifier.
- The additional 180° phase shift is provided by an RC ladder network.
- It can be used for very low frequencies and provides good frequency stability.



A phase shift of 180° is obtained at a frequency f , given by

$$f = \frac{1}{2\pi CR\sqrt{6}}$$

At this frequency the gain of the network is $\frac{V_o}{V_i} = -\frac{1}{29}$


RC Oscillators: Phase shift Oscillator

At node V_2

$$V_2 = V_o + I_3 X_c = V_o + \frac{I_3}{j\omega C}$$

But $I_3 = \frac{V_o}{R}$
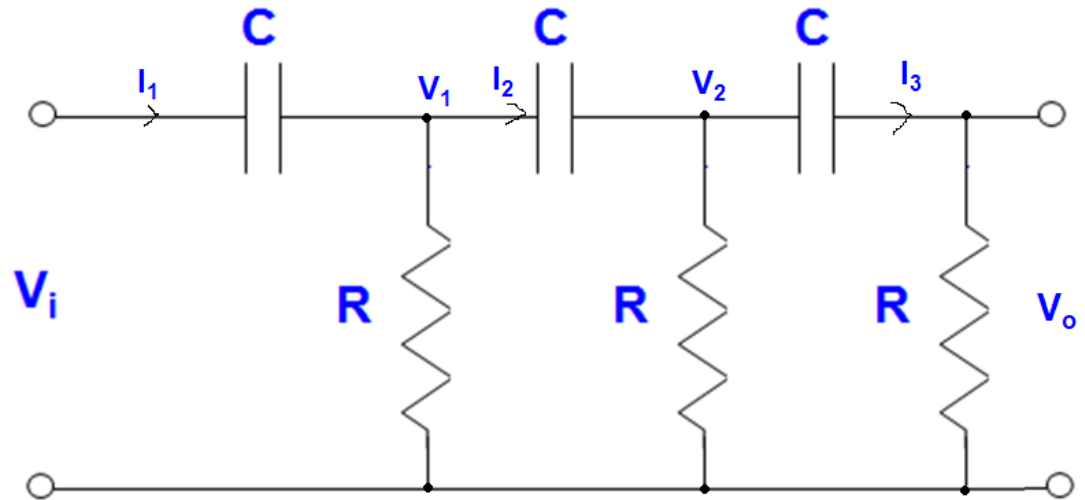
$$V_2 = V_o \left(1 + \frac{1}{j\omega CR} \right)$$



$$I_2 = I_3 + \frac{V_2}{R} = \frac{V_o}{R} + \frac{V_o}{R} \left(1 + \frac{1}{j\omega CR} \right)$$

$$I_2 = \frac{V_o}{R} \left(2 + \frac{1}{j\omega CR} \right)$$

At node V_1

$$V_1 = V_2 + \frac{I_2}{j\omega C} = V_o \left(1 + \frac{3}{j\omega CR} - \frac{1}{\omega^2 C^2 R^2} \right)$$

RC Oscillators: Phase shift Oscillator

$$V_1 = V_2 + \frac{I_2}{j\omega C} = V_o \left(1 + \frac{3}{j\omega R} - \frac{1}{\omega^2 C^2 R^2} \right)$$

$$I_1 = I_2 + \frac{V_1}{R} = \frac{V_o}{R} \left(3 + \frac{4}{j\omega R} - \frac{1}{\omega^2 C^2 R^2} \right)$$

$$V_i = V_1 + \frac{I_1}{j\omega C} = V_o \left(1 + \frac{6}{j\omega R} - \frac{5}{\omega^2 C^2 R^2} - \frac{1}{j\omega^3 C^3 R^3} \right)$$

Output voltage should be real hence imaginary part equal to zero.


$$\frac{6}{j\omega R} - \frac{1}{j\omega^3 C^3 R^3} = 0$$

$$6\omega^2 C^2 R^2 = 1$$

$$\omega = \frac{1}{RC\sqrt{6}}$$

At this frequency: $V_i = -29 V_o$ therefore, $A_v = -29$

RC Oscillators: Wien Bridge Oscillator

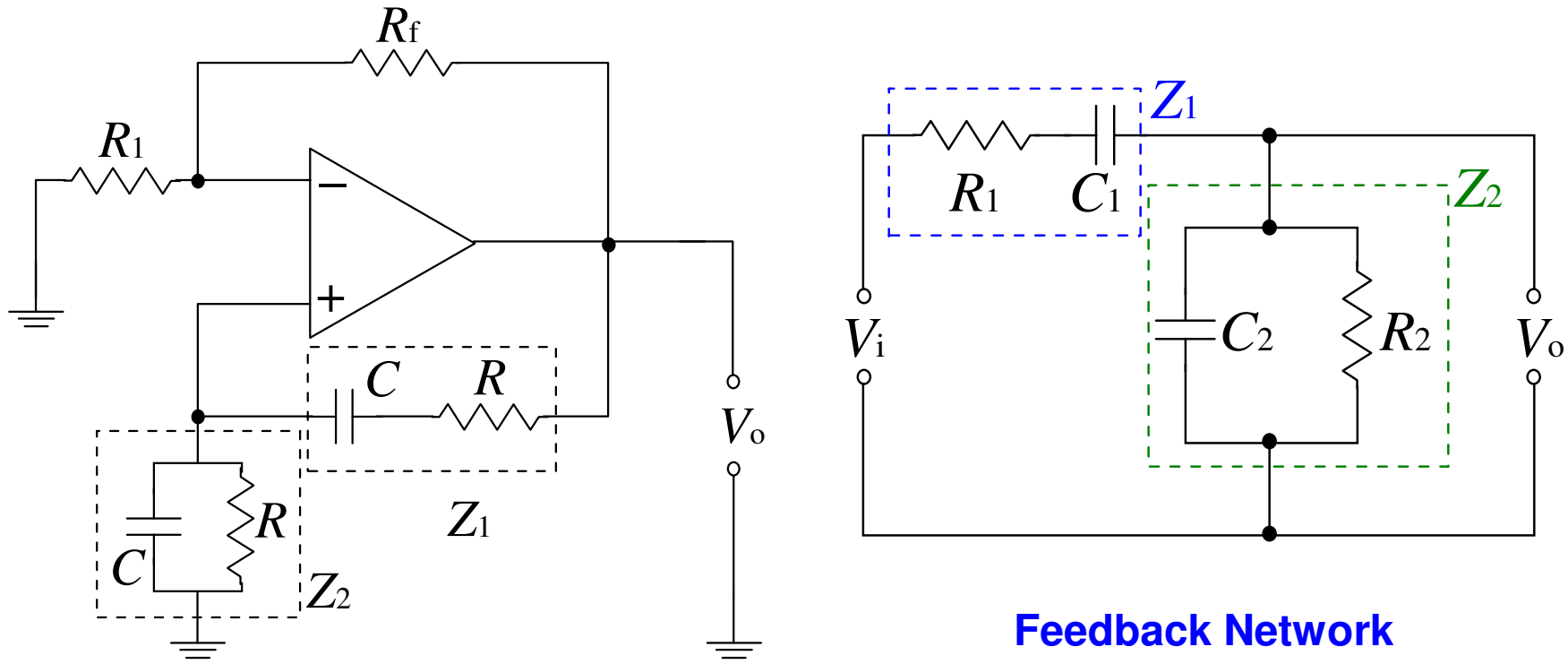

➤ Feedback network is a lead-lag circuit where R_1 , C_1 form the lag portion and R_2 , C_2 form the lead portion. Thus feedback network provides 0° phase shift.

RC Oscillators: Wien Bridge Oscillator

Let $X_{C1} = \frac{1}{\omega C_1}$ $X_{C2} = \frac{1}{\omega C_2}$ and

$$Z_1 = R_1 - jX_{C1}$$


$$Z_2 = \left[\frac{1}{R_2} + \frac{1}{-jX_{C2}} \right]^{-1} = \frac{-jR_2X_{C2}}{R_2 - jX_{C2}}$$

Therefore, the feedback factor,

$$\beta = \frac{V_o}{V_i} = \frac{Z_2}{Z_1 + Z_2} = \frac{(-jR_2X_{C2} / R_2 - jX_{C2})}{(R_1 - jX_{C1}) + (-jR_2X_{C2} / R_2 - jX_{C2})}$$

$$\beta = \frac{-jR_2X_{C2}}{(R_1 - jX_{C1})(R_2 - jX_{C2}) - jR_2X_{C2}}$$
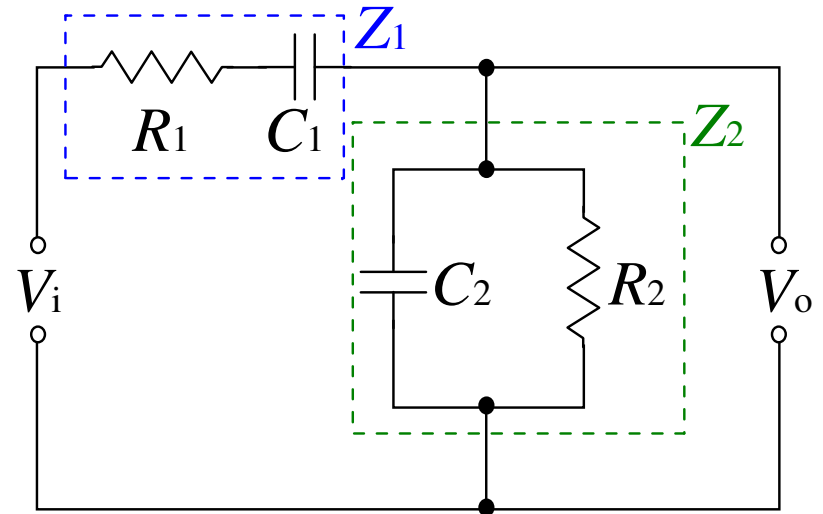
$$\beta = \frac{R_2X_{C2}}{R_1X_{C2} + R_2X_{C1} + R_2X_{C2} + j(R_1R_2 - X_{C1}X_{C2})}$$



RC Oscillators: Wien Bridge Oscillator

For **Barkhausen Criterion**, imaginary part = 0, $R_1 R_2 - X_{C1} X_{C2} = 0$

$$R_1 R_2 = \frac{1}{\omega C_1} \frac{1}{\omega C_2} \quad \boxed{\omega = 1 / \sqrt{R_1 R_2 C_1 C_2}}$$

Supposing, $R_1 = R_2 = R$ and $X_{C1} = X_{C2} = X_C$,



$$\beta = \frac{R X_C}{3 R X_C + j(R^2 - X_C^2)}$$

At this frequency: $\beta = 1 / 3$ and phase shift = 0°



Due to **Barkhausen Criterion**, gain $A_v \beta = 1$

Where A_v : Gain of the amplifier
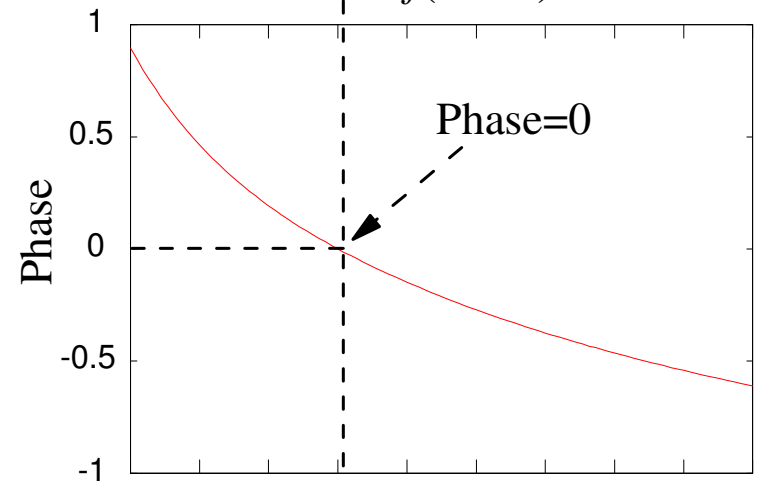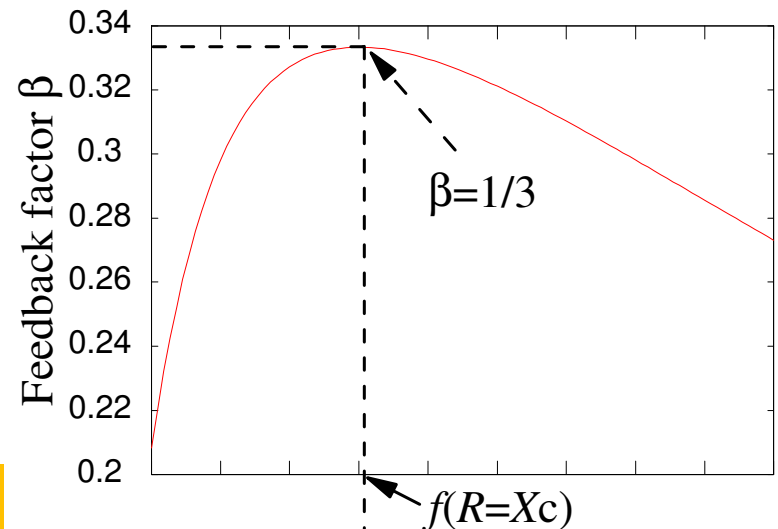
$$A_v \beta = 1 \Rightarrow A_v = 3 = 1 + \frac{R_f}{R_1} \quad \boxed{\frac{R_f}{R_1} = 2}$$



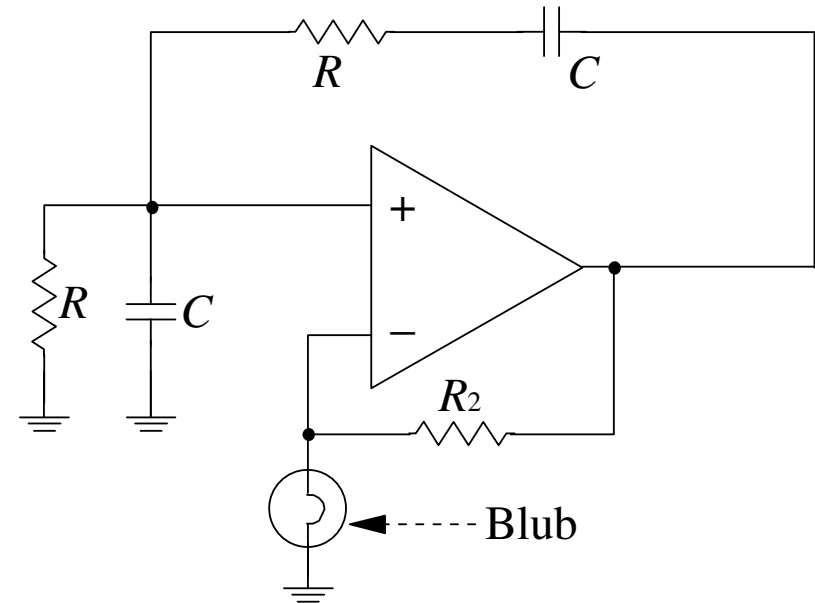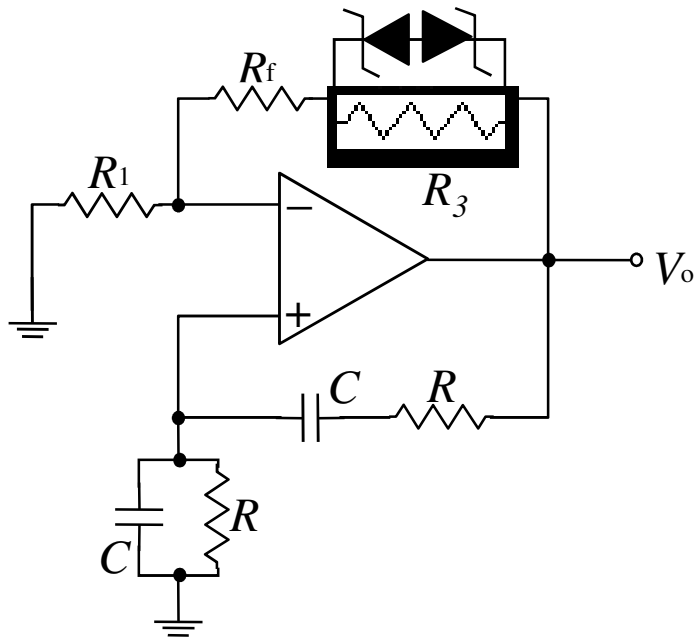Stabilization method for Wien Bridge Oscillator



When dc power is first applied, both zener diode is off.

$$A_v = 1 + \frac{R_f + R_3}{R_1} = 3 + \frac{R_3}{R_1} \quad \text{Because} \quad \frac{R_f}{R_1} = 2$$

Initially, a small +ve feedback signal develops from noise or turn-on transients. This feedback signal is amplified and continually reinforced, resulting in a buildup of the output voltage. When the output voltage reaches the zener breakdown voltage, zener diode conducts and effectively short out R_3 and thus lowers the close loop voltage gain to 3.