

Analog Electronics

Course No: AE-2

Lec: LC & Crystal Oscillators


Course Instructor: Dr. Arka Roy
Dept of ECE, PDEU




PDEU PANDIT
DEENDAYAL
ENERGY
UNIVERSITY

Formerly **Pandit Deendayal Petroleum University**



LC Tank Circuit:

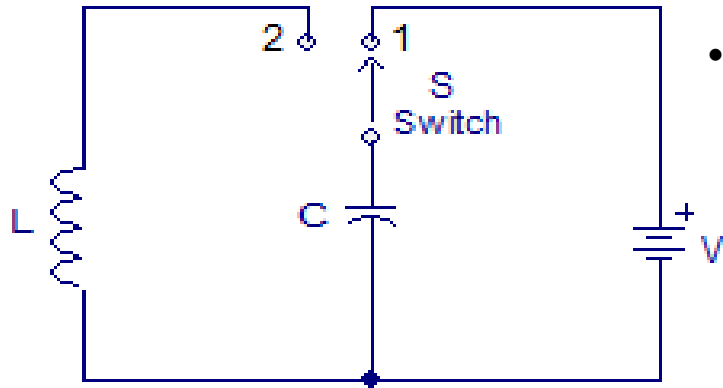

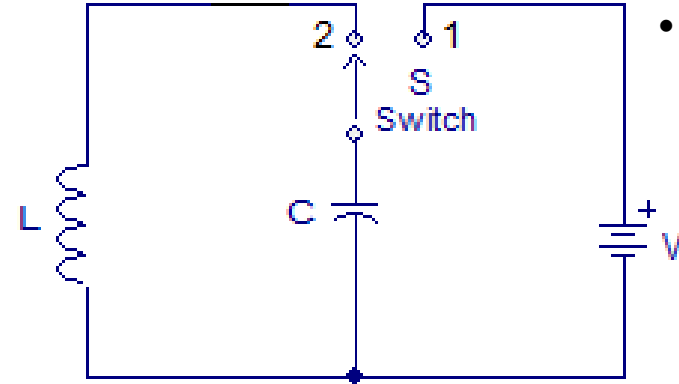- Initially capacitor is not charged:
 $V_c(0^-) = 0$



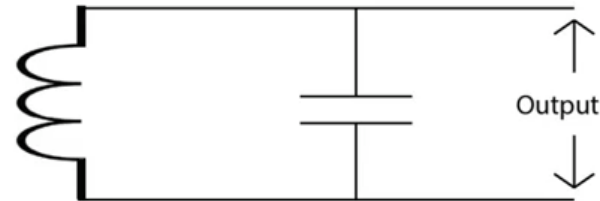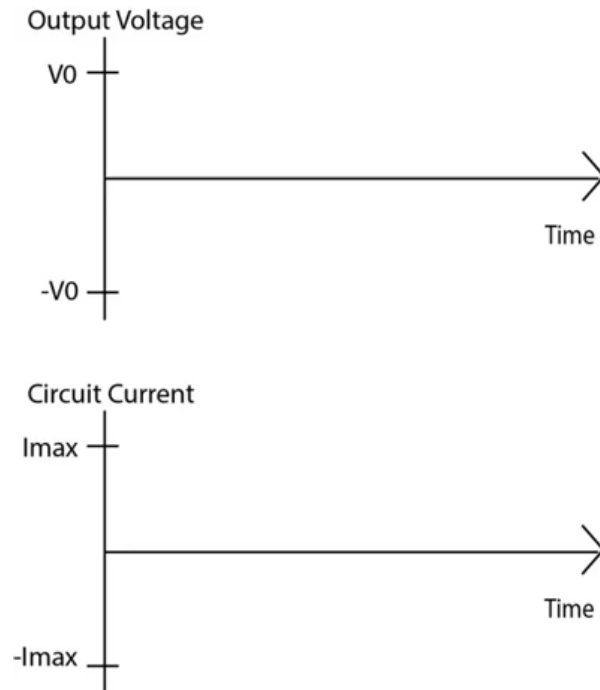
- Continuous charging and discharging of capacitor and inductor



Tuned Oscillators Circuits: LC Oscillators

Tuned oscillators use a parallel LC resonant circuit (LC tank) to provide the oscillations.

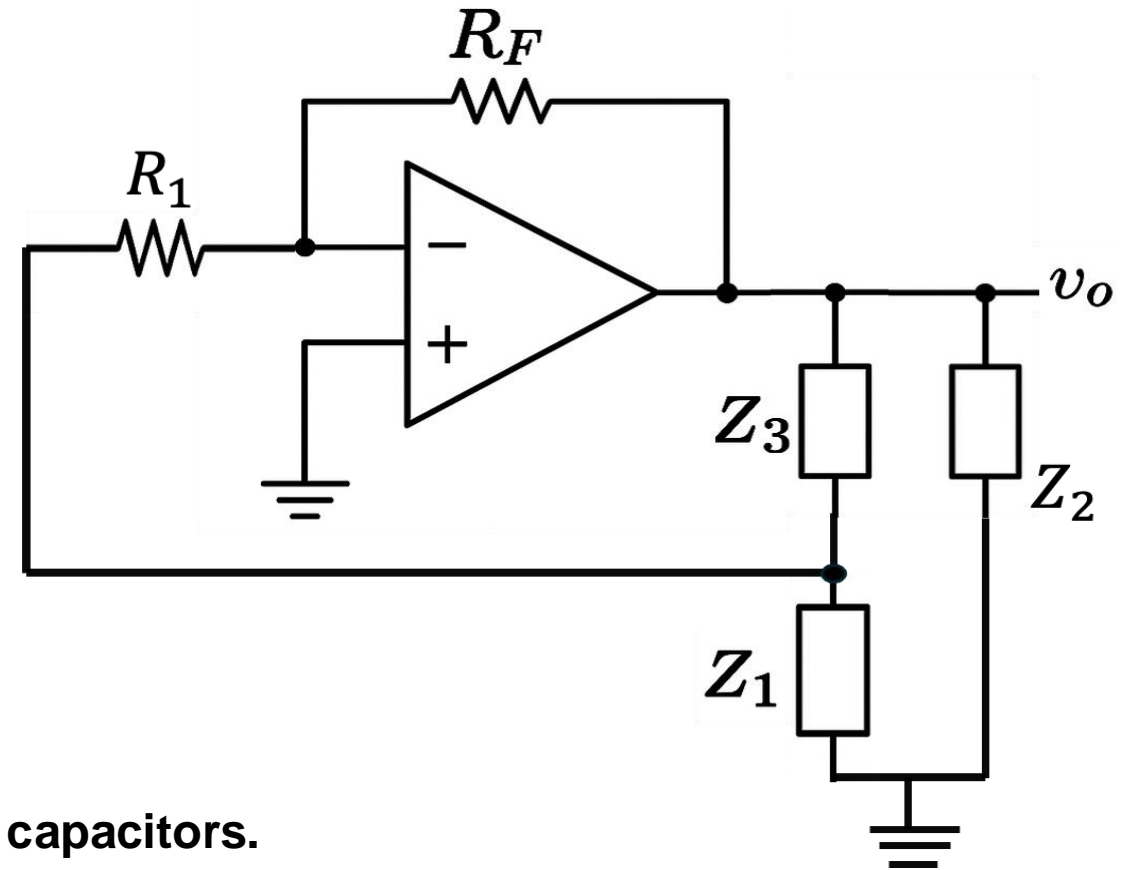- The frequency selection network (Z_1 , Z_2 and Z_3) provides a phase shift of 180°
- Output voltage is developed across Z_2 and feedback voltage is developed across Z_1 .
- The amplifier provides additional shift of 180°




There are two common types:


Colpitts—The resonant circuit is an inductor and two capacitors.

Hartley—The resonant circuit is a tapped inductor or two inductors and one capacitor.

Generalized LC Oscillator:


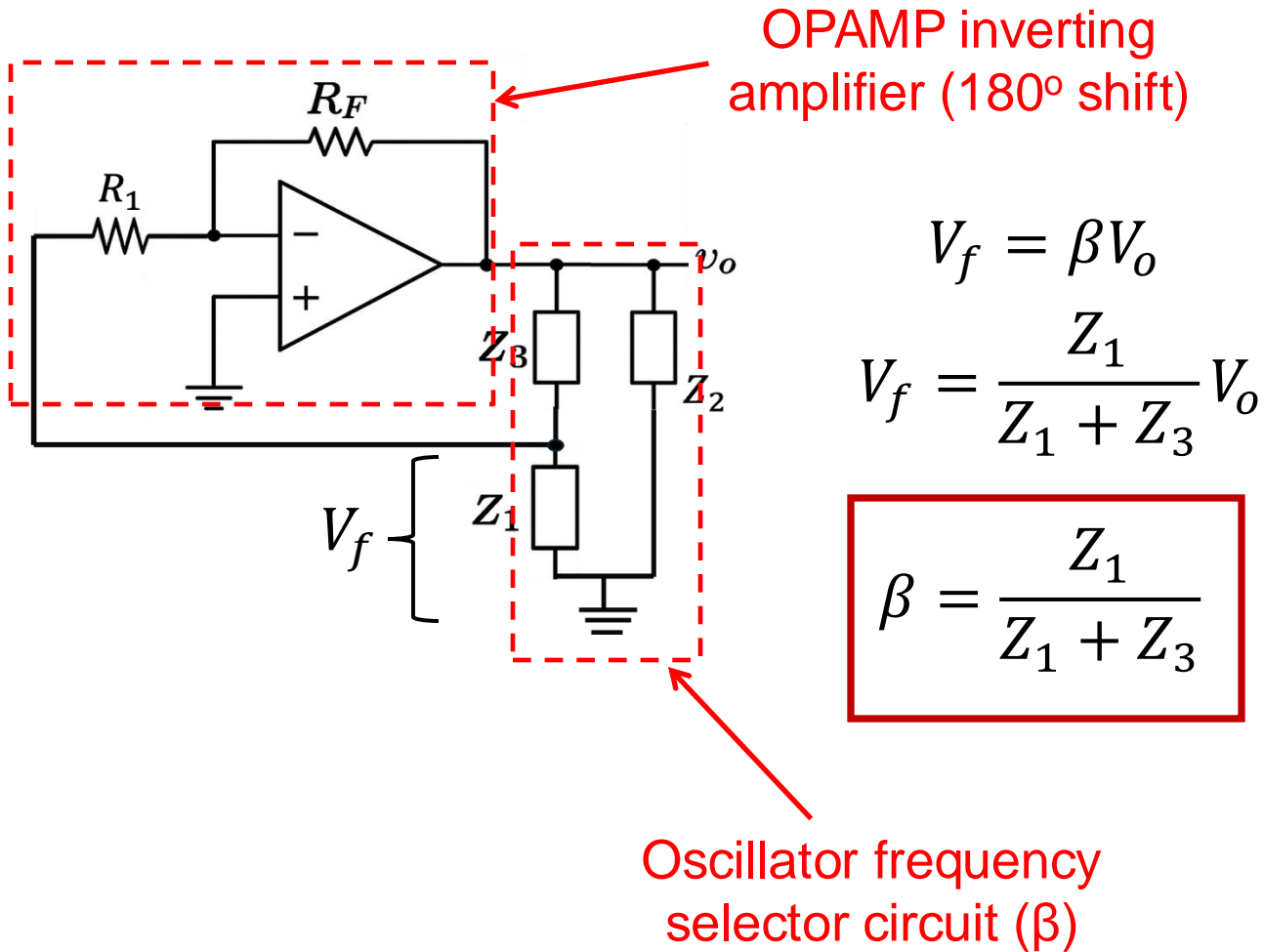


OPAMP's internal ckt:

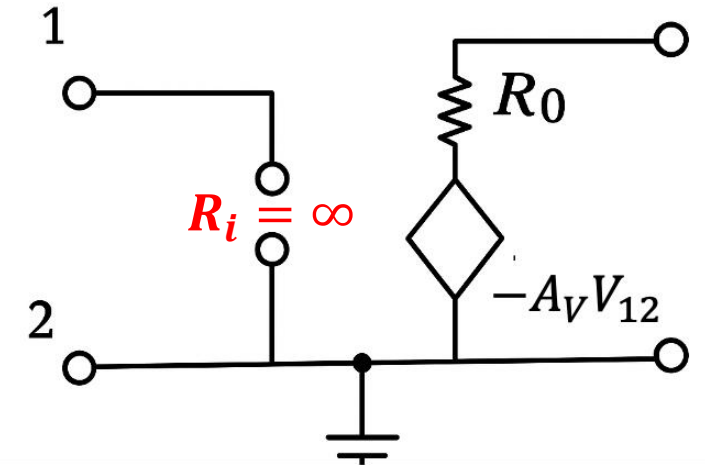

- $R_i = \infty$ (very high so we can reject)
- But R_o is finite but low

Generalized LC Oscillator:

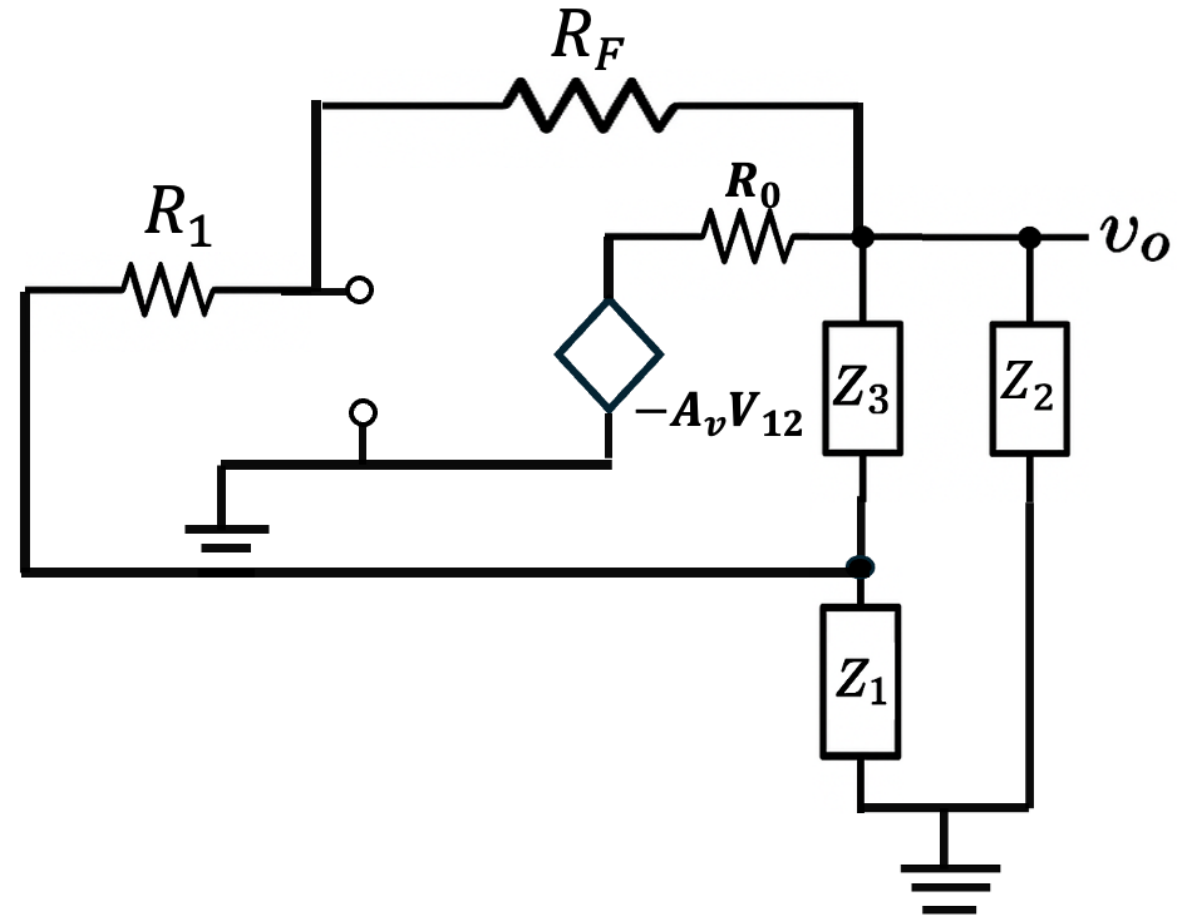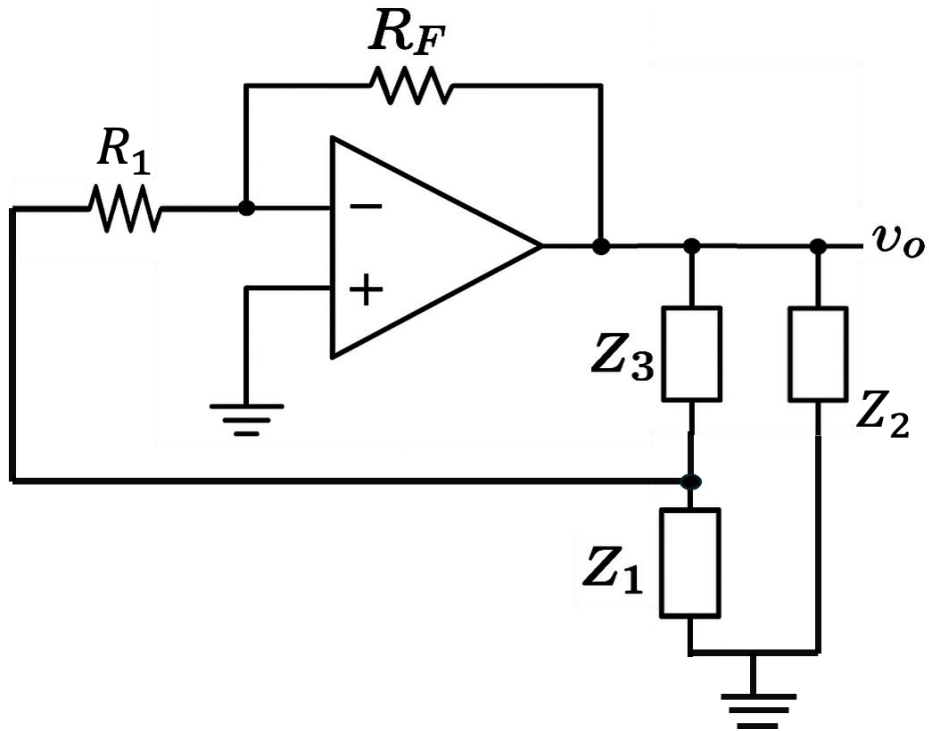

$$V_0 = -A_v V_{12} \times \frac{Z_l}{Z_l + R_0}$$

$$Z_l = Z_2 || (Z_1 + Z_3)$$

$$= \frac{Z_2 \times (Z_1 + Z_3)}{Z_1 + Z_3 + Z_2}$$

$$A = \frac{V_0}{V_{12}} = -A_v \times \frac{Z_l}{Z_l + R_0}$$

$$A = \frac{-A_v \times Z_2 \times (Z_1 + Z_3)}{R_0 \times (Z_1 + Z_3 + Z_2) + Z_2 \times (Z_1 + Z_3)}$$

$$A = \frac{-A_v \times Z_2 \times (Z_1 + Z_3)}{R_0 \times (Z_1 + Z_3 + Z_2) + Z_2 \times (Z_1 + Z_3)}$$

$$\beta = \frac{Z_1}{Z_1 + Z_2}$$

$$A\beta = \frac{-A_v \times Z_2 \times Z_1}{R_0 \times (Z_1 + Z_3 + Z_2) + Z_2 \times (Z_1 + Z_3)}$$

Let $Z_1, Z_2, Z_3 = jX_1, jX_2, jX_3$;
 where $X = \omega L$, or $(-\frac{1}{\omega C})$

$$A\beta = \frac{A_v \times X_2 \times X_1}{jR_0 \times (X_1 + X_3 + X_2) - X_2 \times (X_1 + X_3)}$$

Aβ should be equal for sustained oscillation:

$$jR_0 \times (X_1 + X_3 + X_2) = 0$$


$$\Rightarrow (X_1 + X_3 + X_2) = 0$$

$$A\beta = \frac{A_v \times X_2 \times X_1}{-X_2 \times (X_1 + X_3)}$$

$$A\beta = \frac{A_v \times X_2 \times X_1}{-X_2 \times -X_2} = \frac{A_v \times X_1}{X_2}$$

$$A_v = \frac{X_2}{X_1}$$

Colpitt's Oscillator:

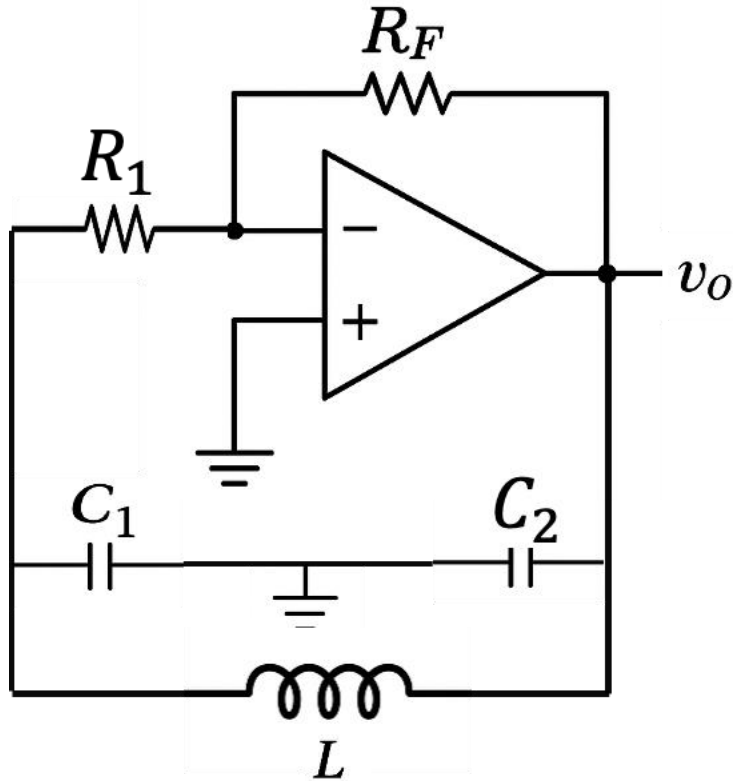

$Z_1, Z_2 \rightarrow$ Capacitors


$Z_3 \rightarrow$ Inductor

Derive relation of f_0 !!

$$\Rightarrow (X_1 + X_3 + X_2) = 0$$

$$-\frac{1}{\omega C_1} + \omega L + -\frac{1}{\omega C_2} = 0$$
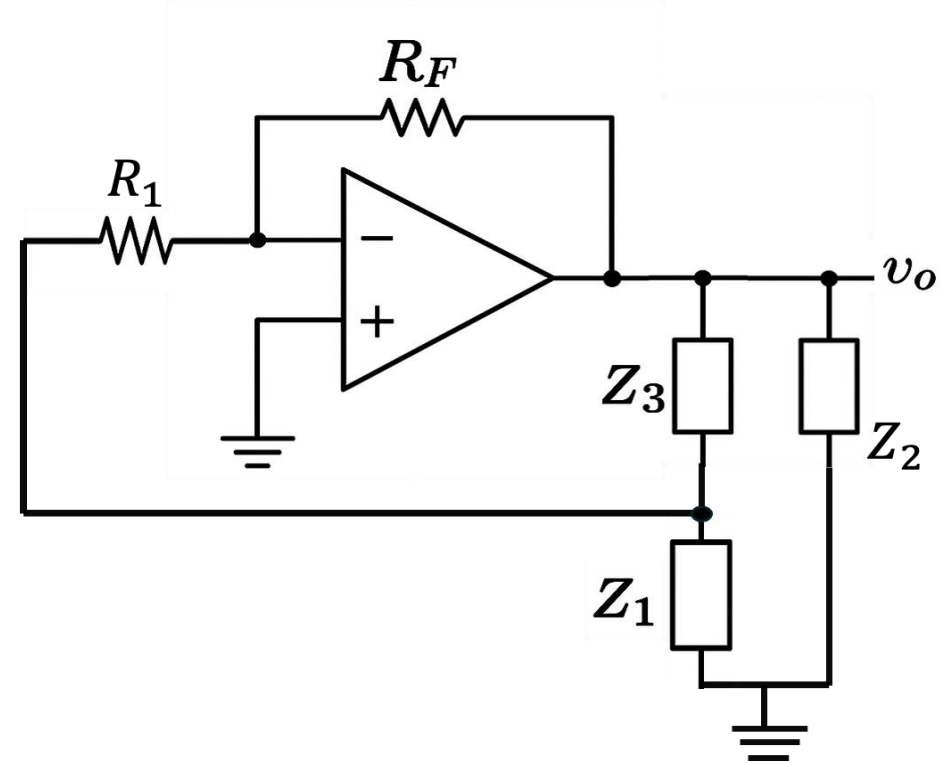
$$f_0 = \frac{1}{2\pi} \sqrt{\frac{(C_1 + C_2)}{LC_1 C_2}}$$



Hartley's Oscillator:

$Z_1, Z_2 \rightarrow$ Inductor


$Z_3 \rightarrow$ Capacitors

Derive relation of f_0 !!

$$\Rightarrow (X_1 + X_2 + X_3) = 0$$

$$\omega L_1 + \omega L_2 + -\frac{1}{\omega C} = 0$$
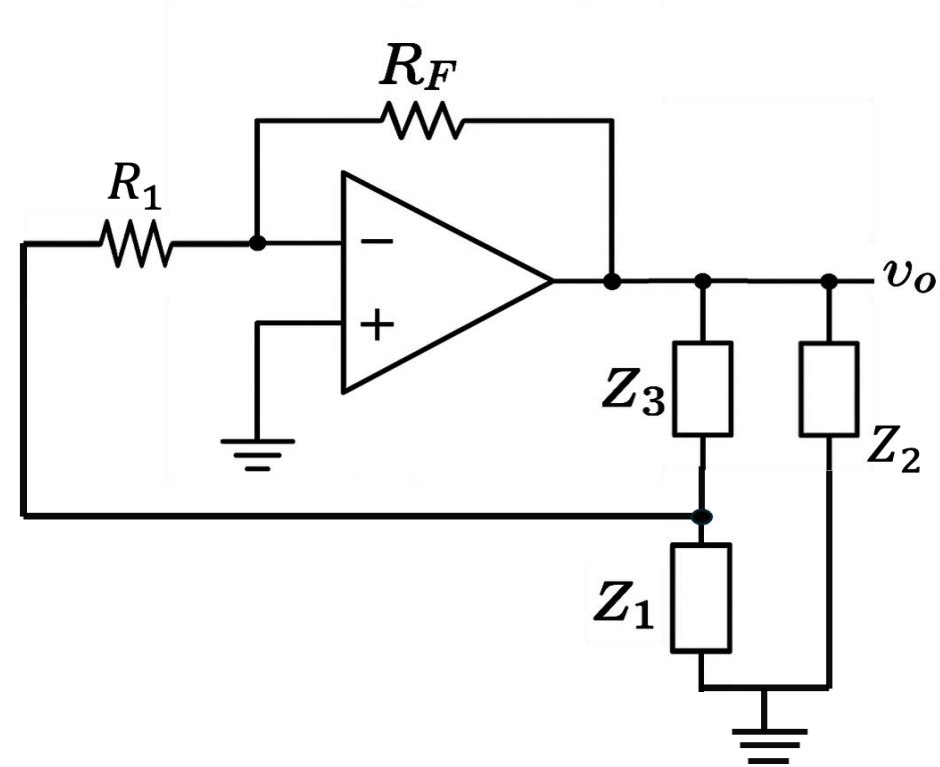
$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{C(L_1 + L_2)}}$$



THE END.

