

# Analog Electronics

**Course No: AE-2**

**Lec: 555 timers and Multi-vibrators**

**Course Instructor: Dr. Arka Roy**  
**Dept of ECE, PDEU**



**PDEU** PANDIT  
DEENDAYAL  
ENERGY  
UNIVERSITY


Formerly **Pandit Deendayal Petroleum University**

## Multivibrators:

- **Multivibrators** are electronic circuits used to generate, store, or process binary signals (i.e., signals with two stable states: HIGH and LOW). They are commonly used in timing applications, pulse generation, and waveform shaping.
- Are of three types: **Astable**, **Mono-stable**, **Bi-stable**

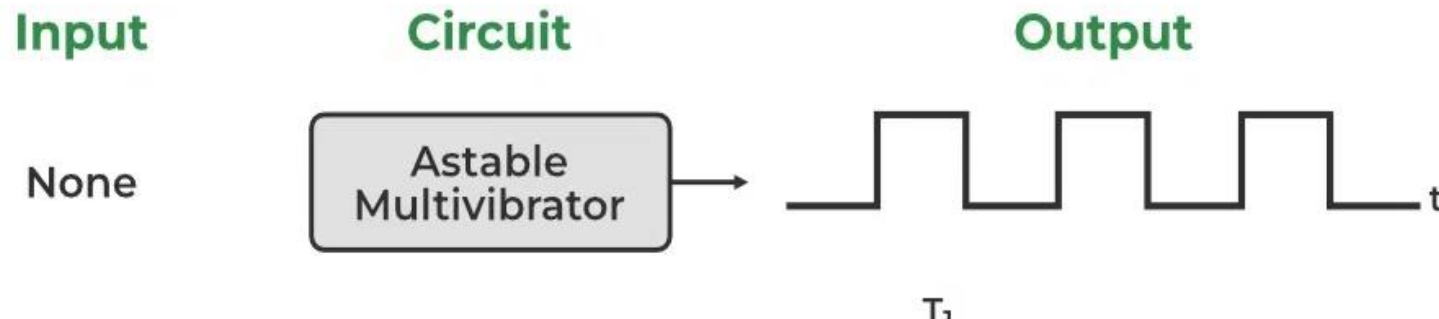
### Astable Multivibrator

- Has **no stable state** → free-running multivibrator.
- Continuously switches between HIGH and LOW states.
- Used as an oscillator or clock generator.



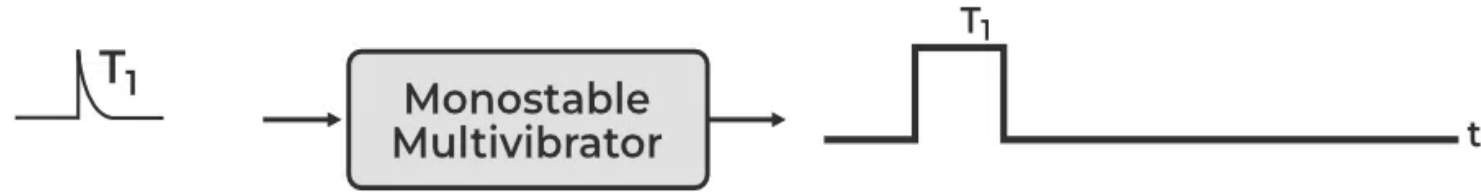
# Mono-stable Multivibrator

- A monostable multivibrator, also called a one-shot multivibrator, is a circuit that responds to an external trigger by producing a single pulse with a set duration.




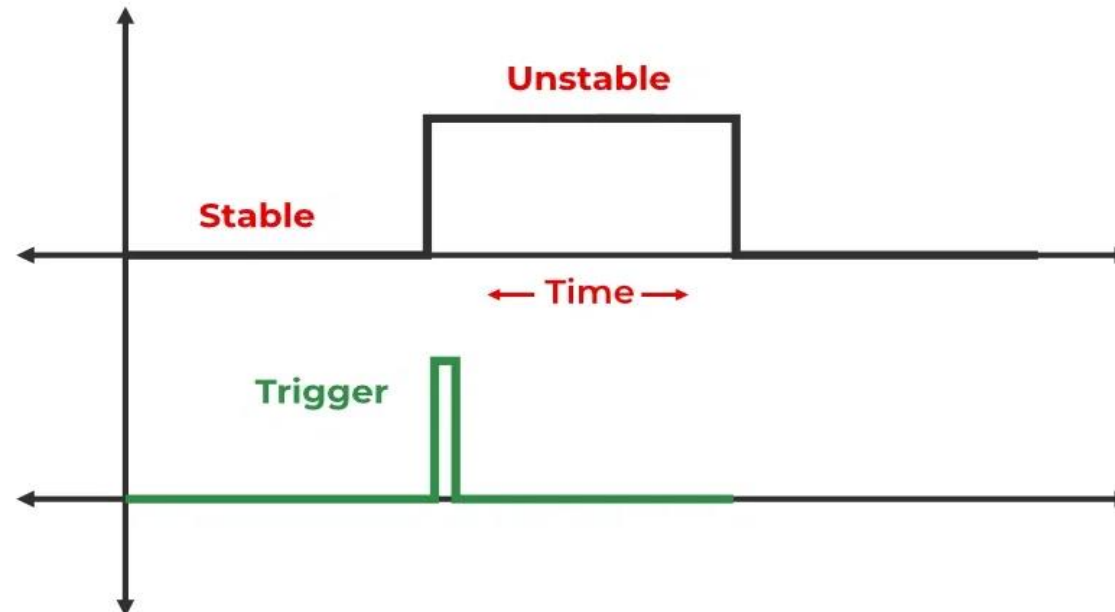- The circuit returns to its stable condition after a certain amount of time and generates a single output pulse.
- By altering the values of the resistors and capacitors in the circuit, the output pulse's duration can be changed.




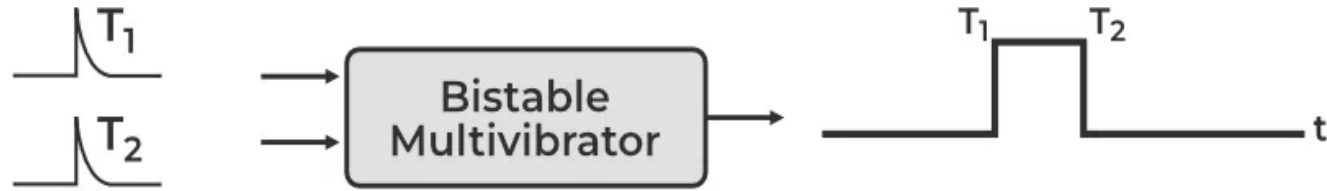
# Bi-stable Multivibrator




- A circuit with two stable states that can alternately exist indefinitely. .



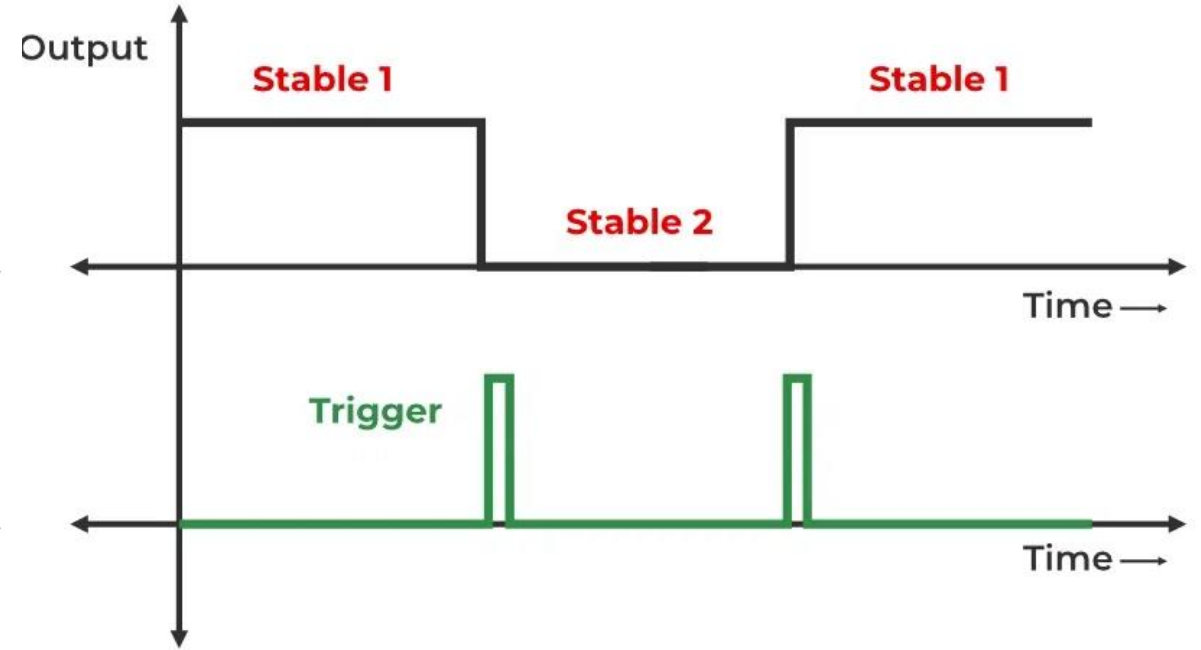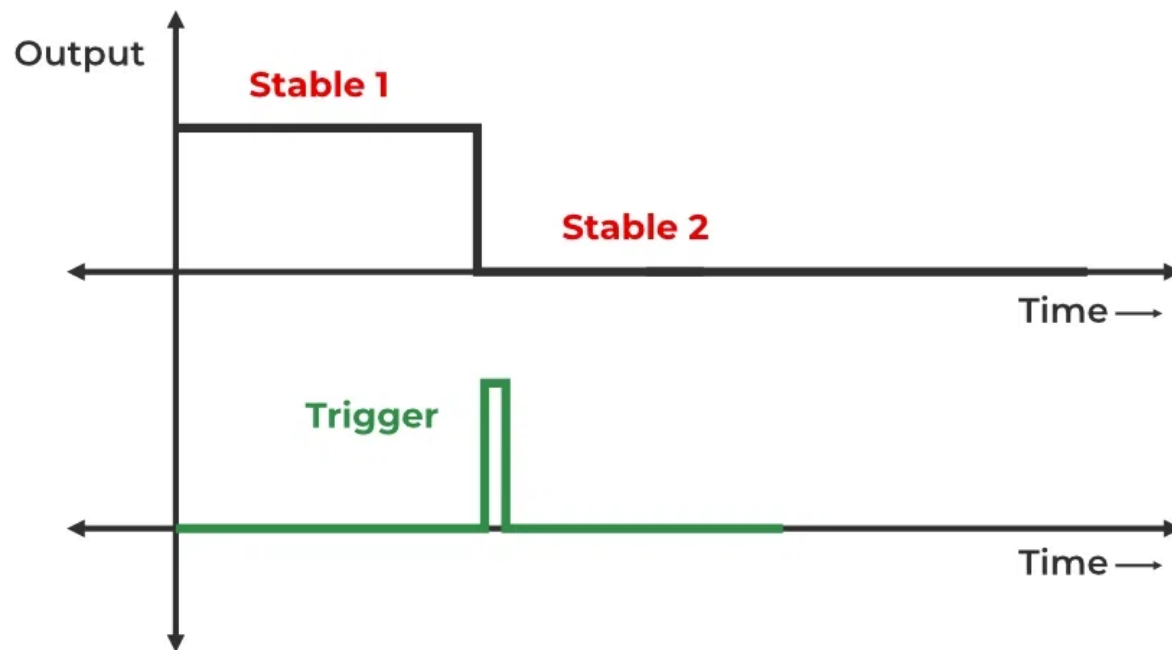- A signal from outside causes it to change from one stable condition to another.
- The circuit will stay in its stable state until another trigger signal enters it.




# 555 Timer:

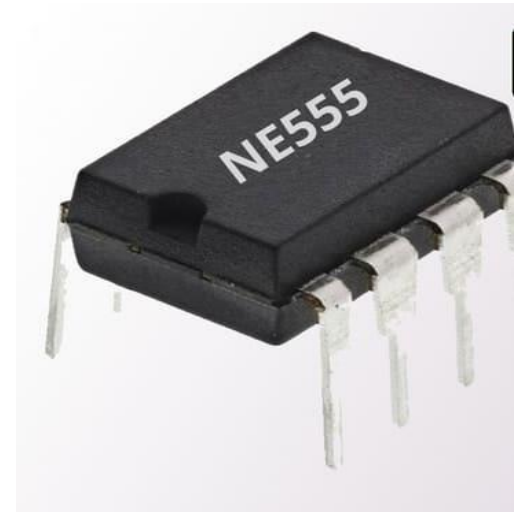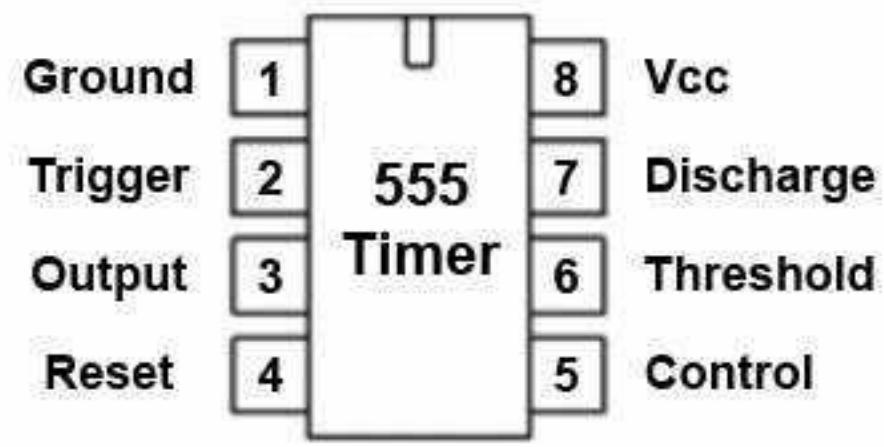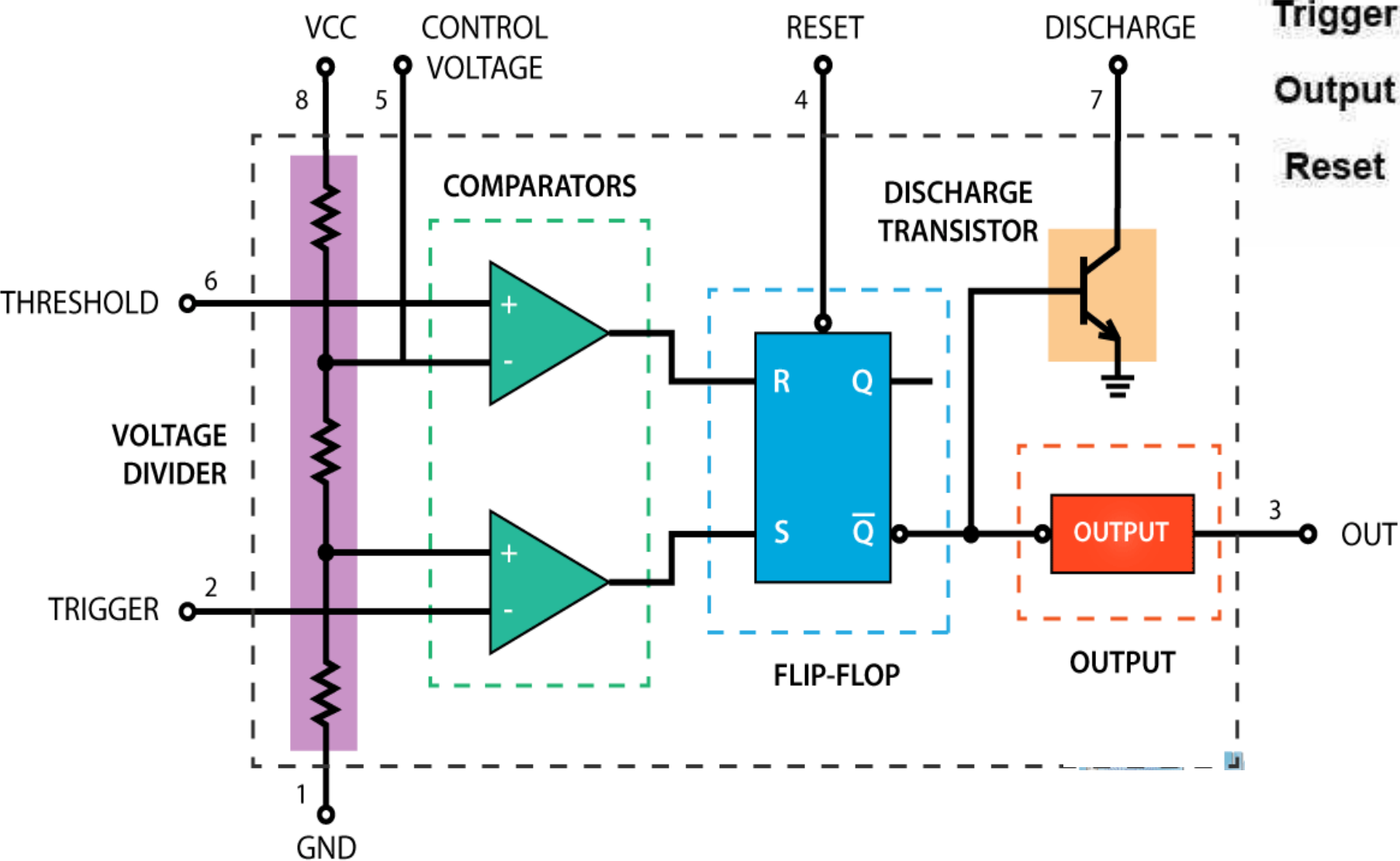

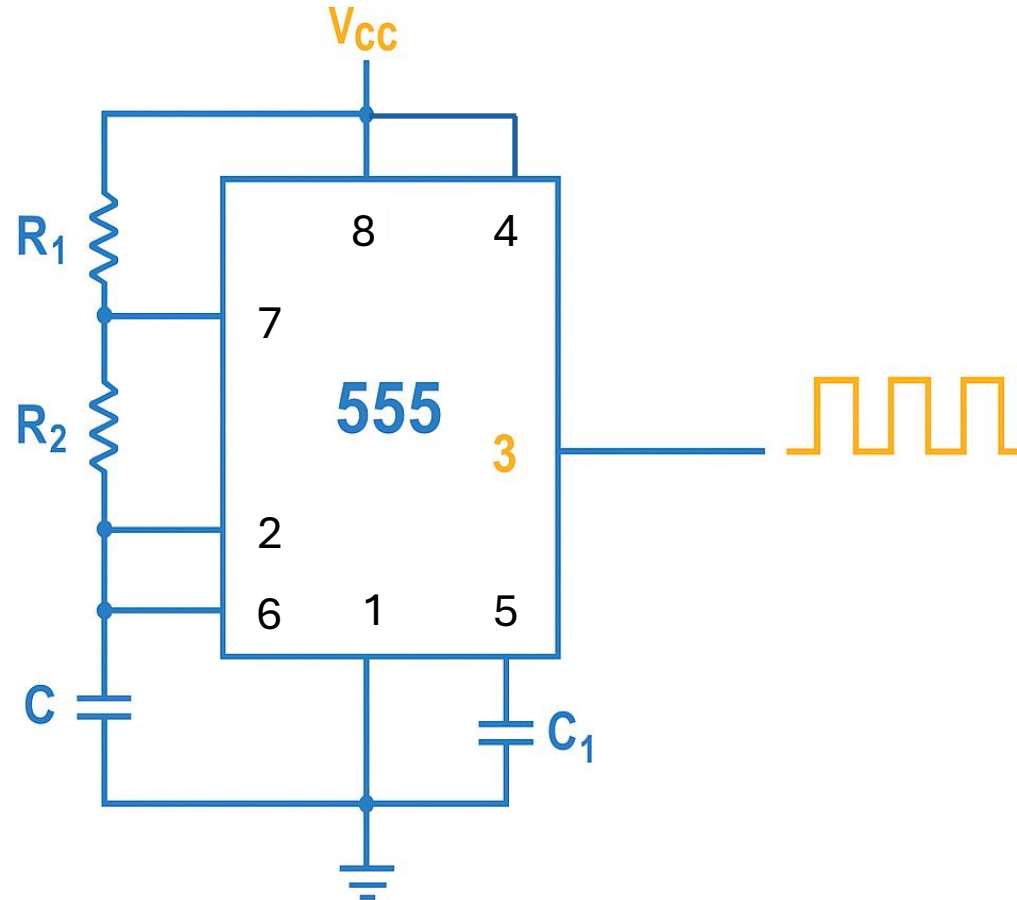
## Astable Multivibrator using 555 timer:


- 1 – Ground
- 2 – Trigger
- 3 – Output
- 4 – Reset
- 5 – Control
- 6 – Threshold
- 7 – Discharge
- 8 – Vcc


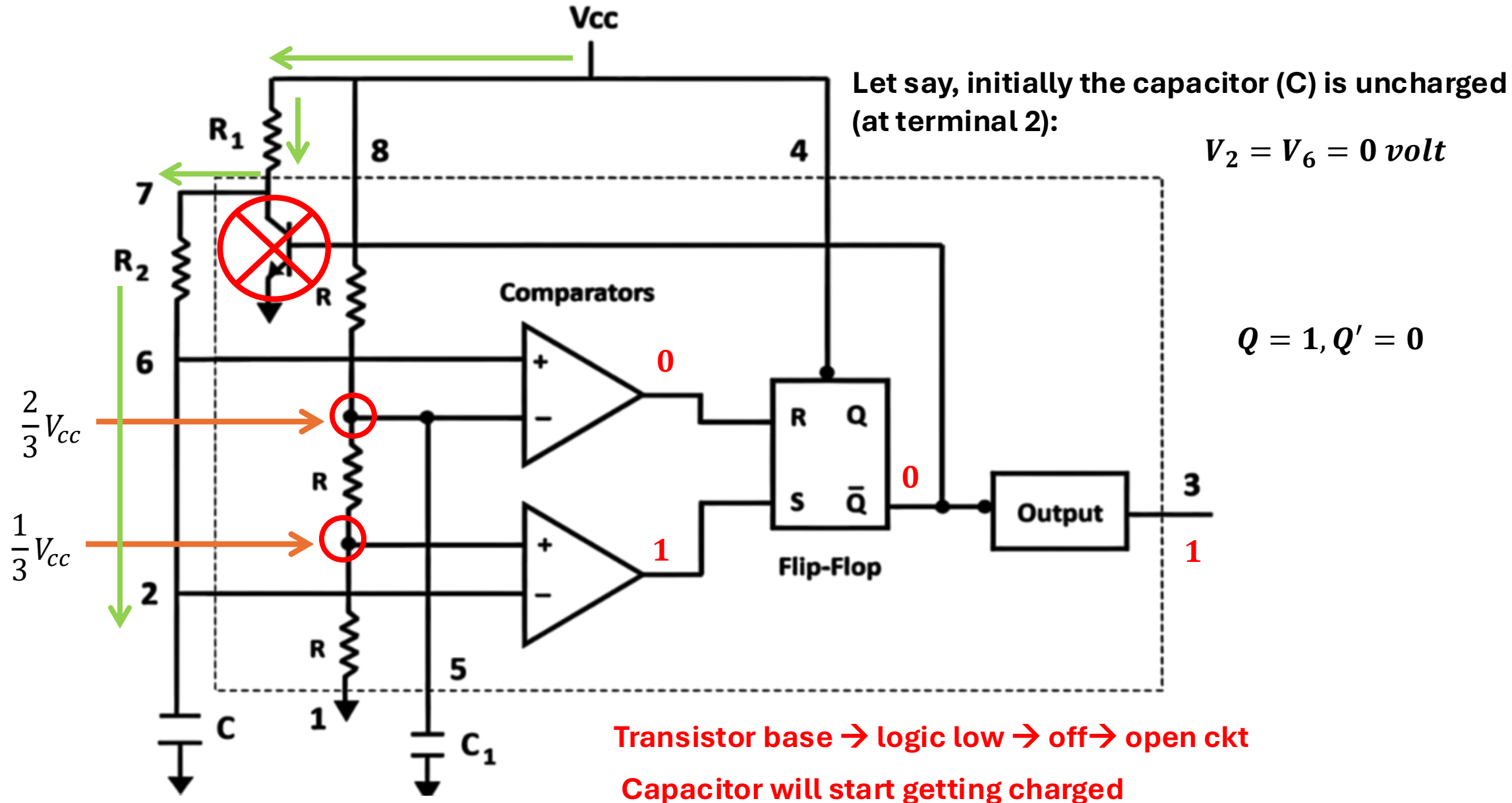
## Astable Multivibrator using 555 timer:



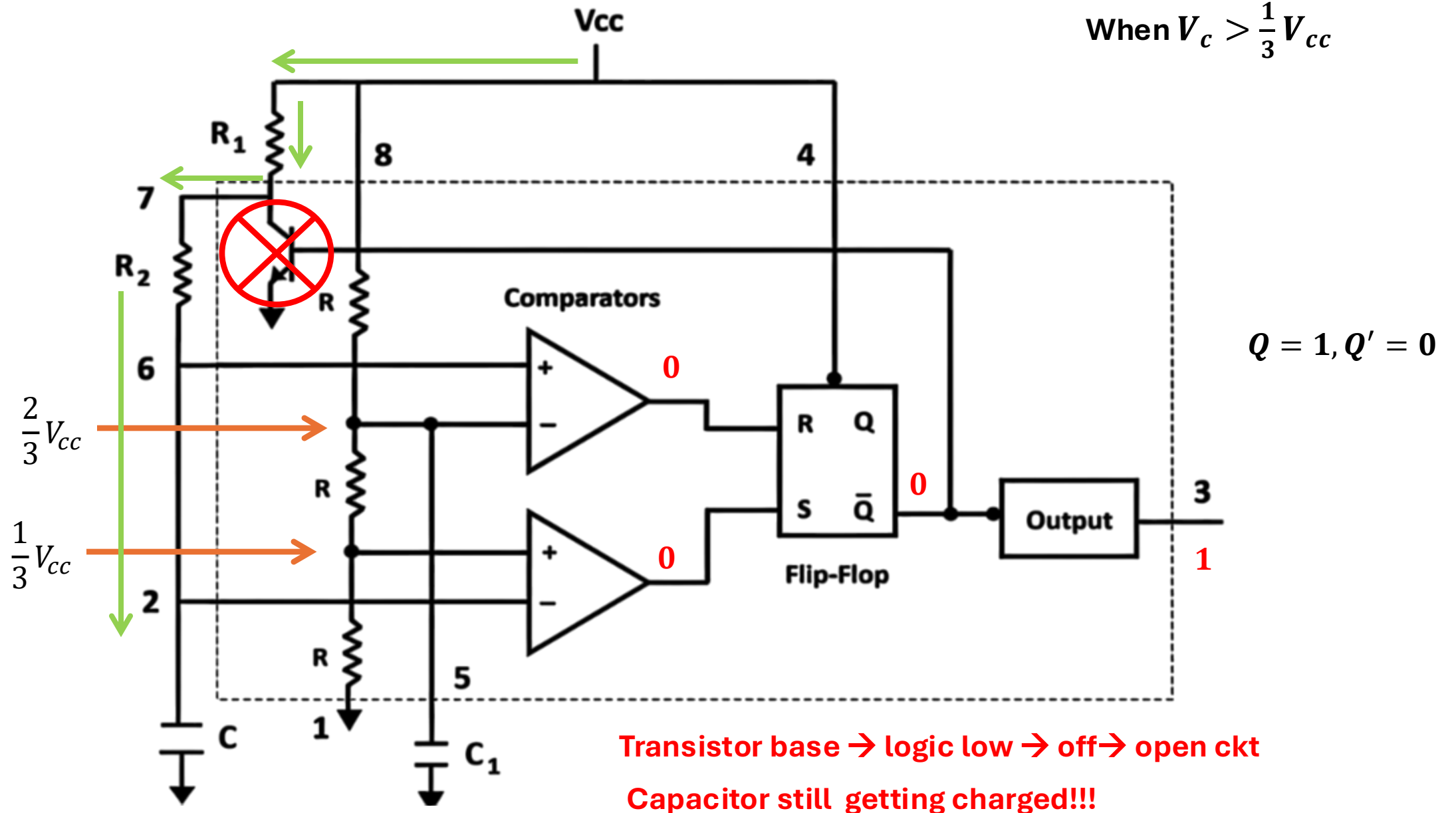
## Astable Multivibrator using 555 timer:





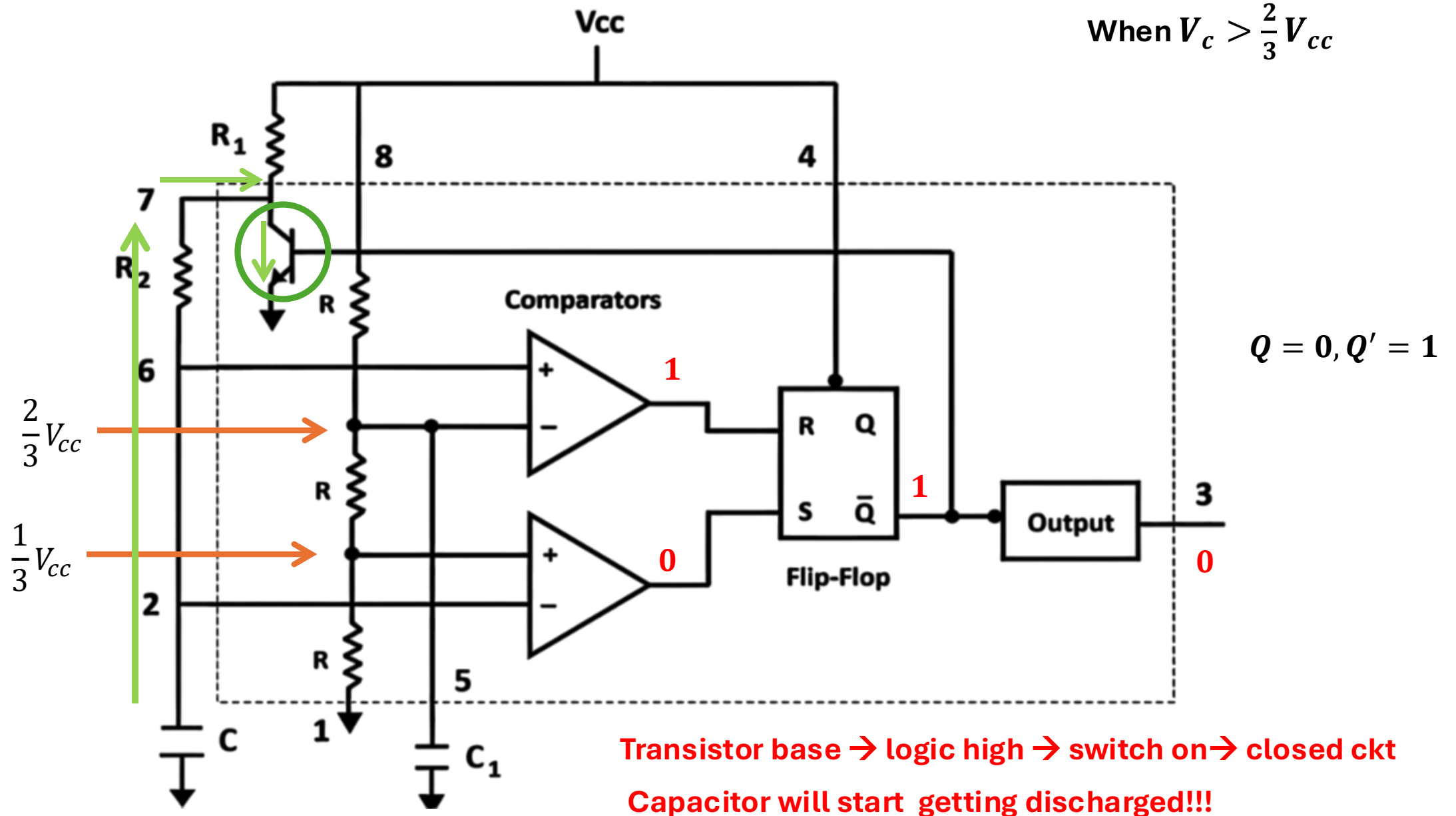
## Astable Multivibrator using 555 timer:



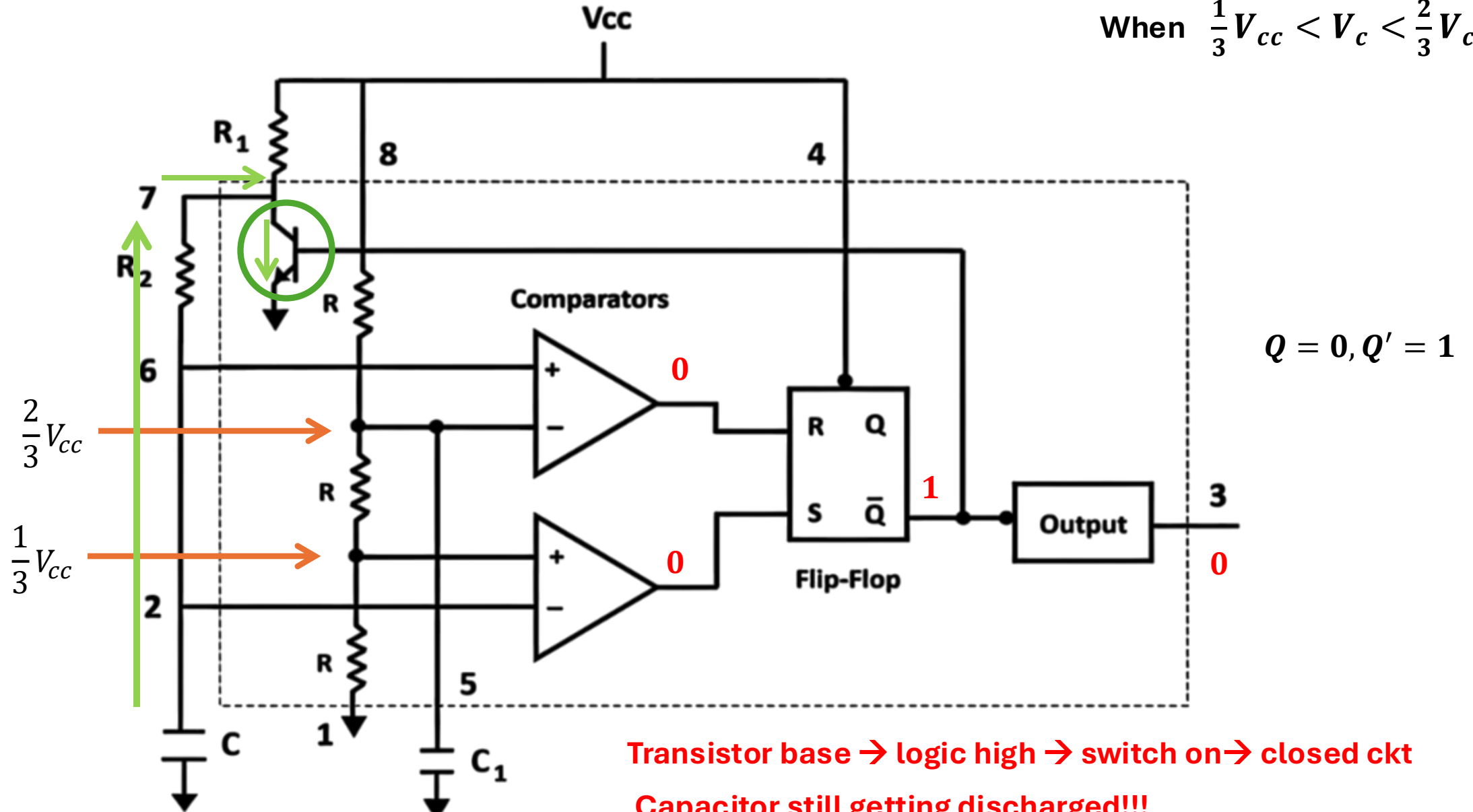
## Astable Multivibrator using 555 timer:


When  $\frac{1}{3}V_{cc} < V_c < \frac{2}{3}V_{cc}$



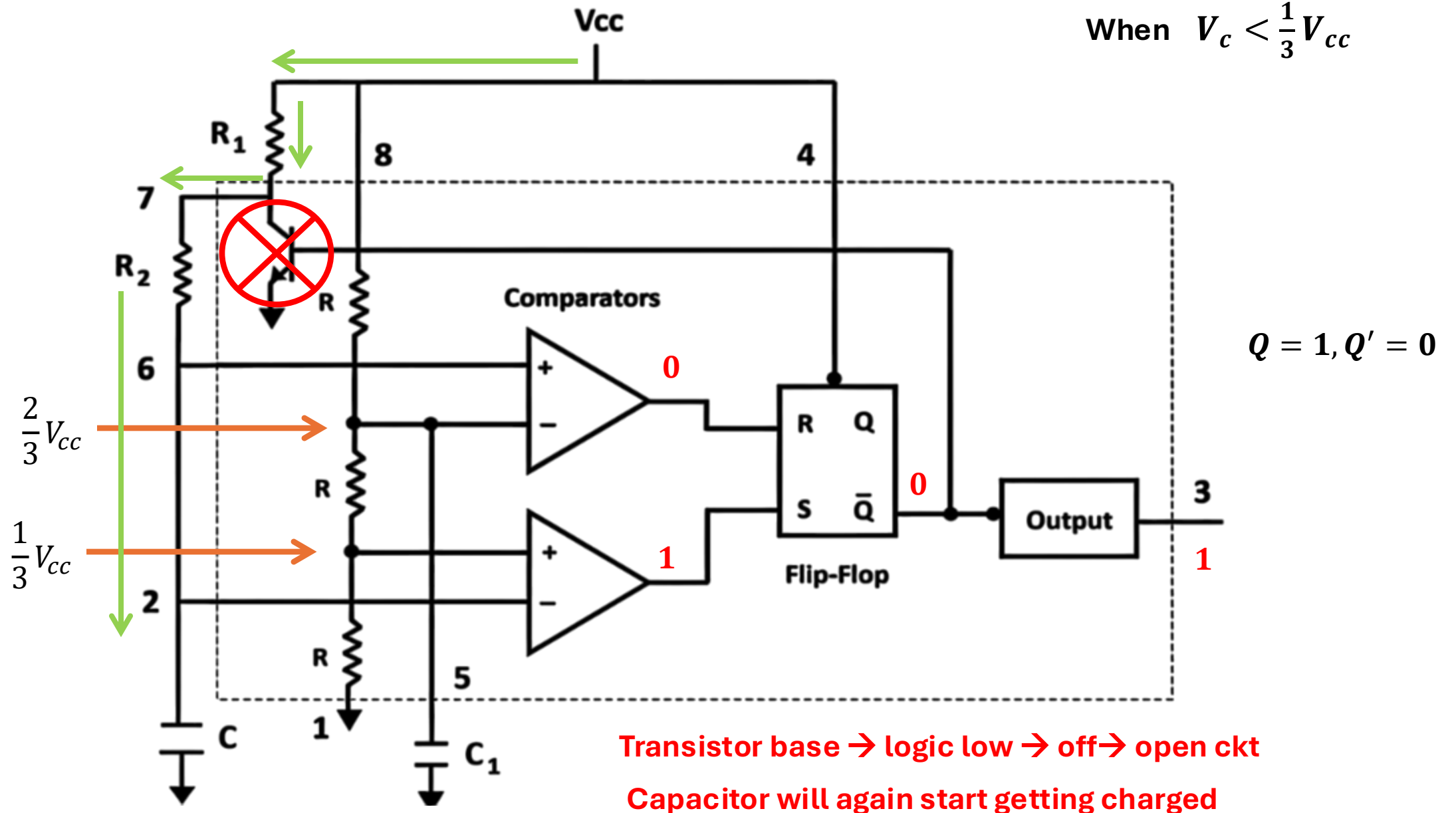
## Astable Multivibrator using 555 timer:


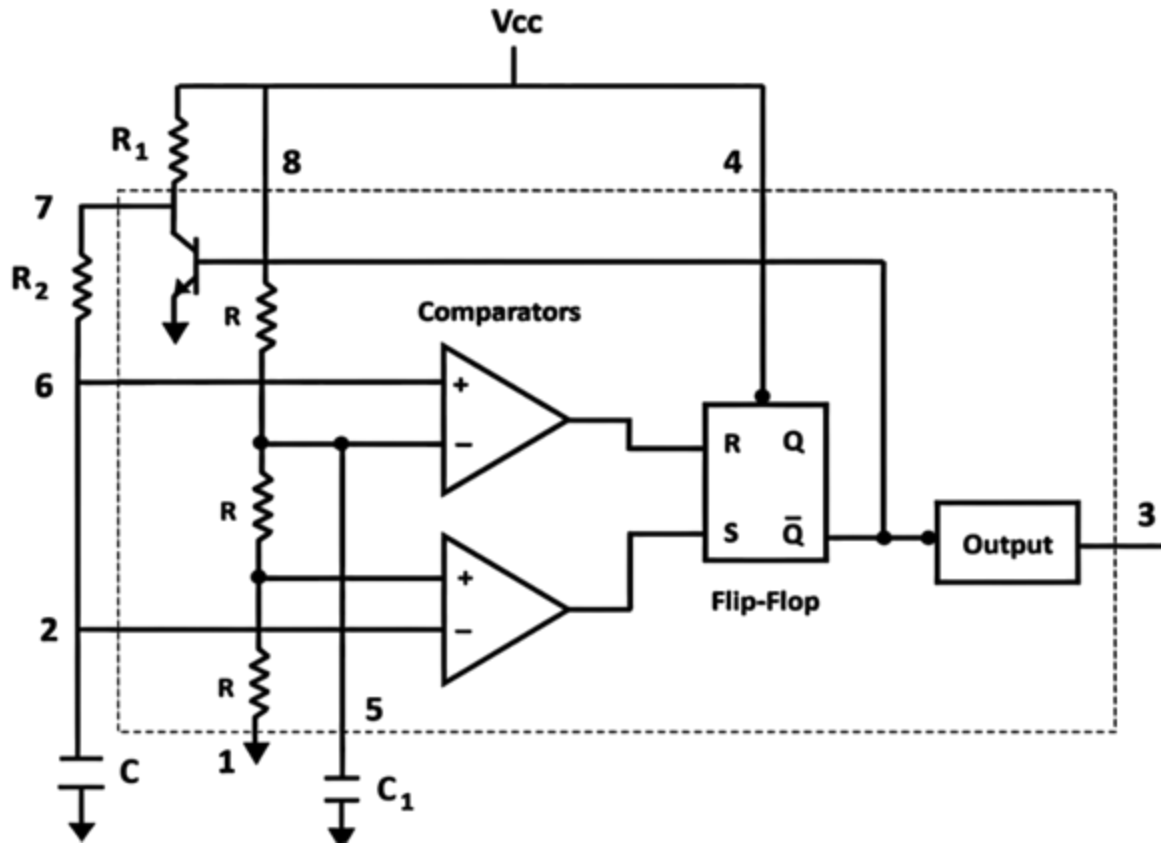
## Astable Multivibrator using 555 timer:



### Let calculate charging time:

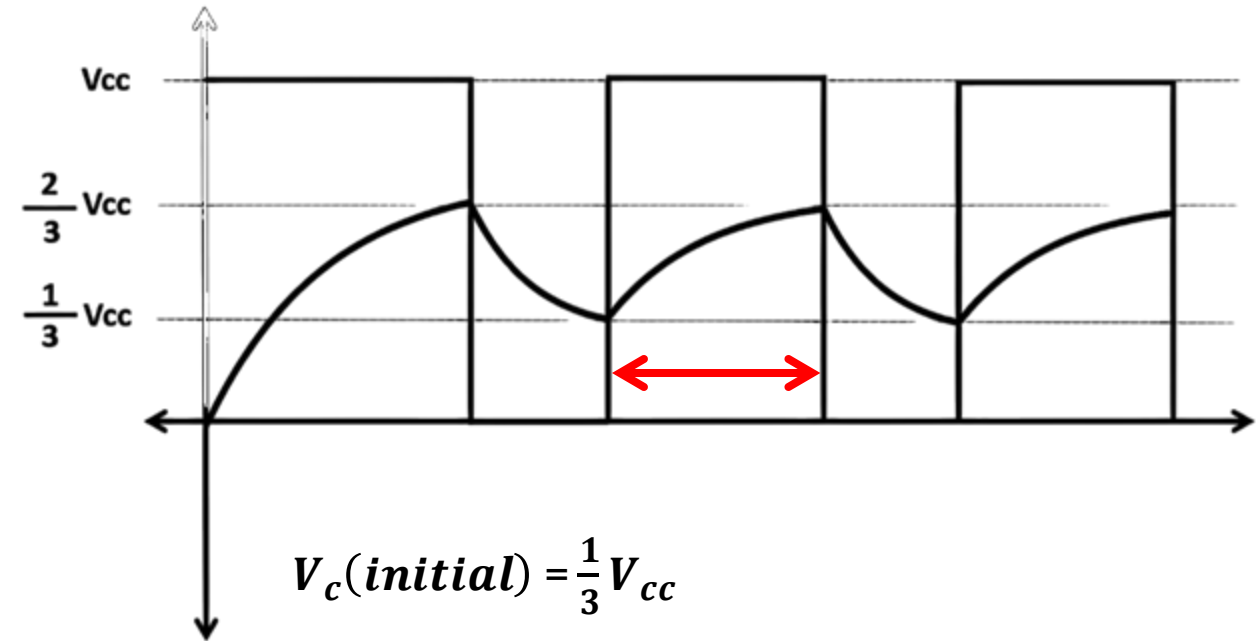

$$V_c(\textit{initial}) = \frac{1}{3} V_{cc}$$

$$V_c(\text{final}) = V_{cc}$$

$$R' = R_1 + R_2$$

**Solve the eq. at end of charging boundary condition!!!**

$$V_c(t) = V_c(\infty) + (V_c(0) - V_c(\infty))e^{\frac{-t}{R'C}}$$

## Astable Multivibrator using 555 timer:


$$V_c(t) = V_c(\infty) + (V_c(0) - V_c(\infty))e^{\frac{-t}{R'C}}$$

$$\frac{2}{3}V_{cc} = V_{cc} + (\frac{1}{3}V_{cc} - V_{cc})e^{\frac{-t_1}{(R_1+R_2) \times C}}$$

$$-\frac{1}{3}V_{cc} = -\frac{2}{3}V_{cc} e^{\frac{-t_1}{(R_1+R_2) \times C}}$$

$$t_1 = \ln(2) \times (R_1 + R_2) \times C$$

Let calculate charging time:

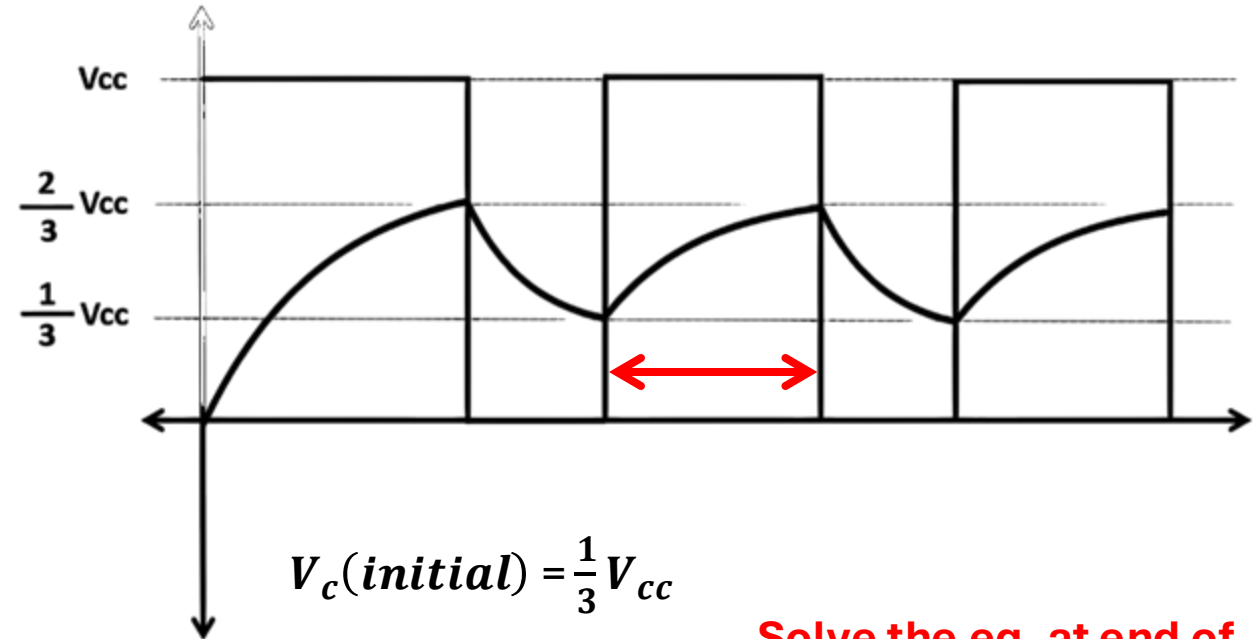

$$V_c(\text{initial}) = \frac{1}{3}V_{cc}$$

$$V_c(\text{final}) = V_{cc}$$

$$R' = R_1 + R_2$$

**Solve the eq. at end of charging boundary condition!!!**

$$t_1 = \ln(2) \times (R_1 + R_2) \times C$$

## Astable Multivibrator using 555 timer:

$$V_c(t) = V_c(\infty) + (V_c(0) - V_c(\infty))e^{\frac{-t}{R'C}}$$

$$\frac{1}{3}V_{cc} = 0 + \left(\frac{2}{3}V_{cc} - 0\right)e^{\frac{-t_2}{R_2 \times C}}$$

$$\frac{1}{3}V_{cc} = \frac{2}{3}V_{cc} e^{\frac{-t_2}{R_2 \times C}}$$

$t_2 = \ln(2) \times R_2 \times C$

**Calculate the time-period of the pulse!!!**

**Let calculate discharging time:**

